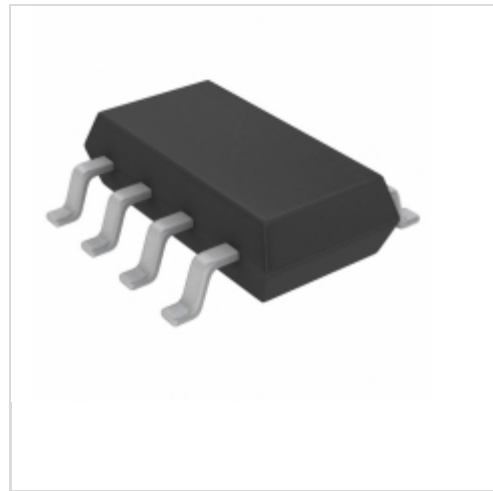


LTC2631AHTS8-LZ12#TRPBF



[Linear Technology / Analog Devices](#)

IC DAC 12BIT VOUT TSOT23-8

Lead free / RoHS Compliant

Integrated Circuits (ICs)

[LTC2631AHTS8-LZ12#TRPBF.pdf](#)

Buy Now

We can supply Linear Technology / Analog Devices LTC2631AHTS8-LZ12#TRPBF, use the request quote form to request LTC2631AHTS8-LZ12#TRPBF price, Linear Technology / Analog Devices Datasheet PDF and lead time. Zeano.com is a professional electronic components distributor. With 3+ Million line items of available electronic components can ship in short lead-time, over 250 thousand part numbers of electronic components in stock for immediately delivery, which may include part number LTC2631AHTS8-LZ12#TRPBF. The price and lead time for LTC2631AHTS8-LZ12#TRPBF depending on the quantity required, availability and warehouse location.

Out Stock

0 pcs

Minimum:1

Multiples:100

Manufacturer lead time 10 weeks

Shopping Process

1

Confirm the product

2

submit the order

3

payment

4

wait for delivery

5

receive the goods

Specifications

Voltage - Supply, Digital:	2.7 V ~ 5.5 V
Voltage - Supply, Analog:	2.7 V ~ 5.5 V
Supplier Device Package:	TSOT-23-8
Settling Time:	4.1µs (Typ)
Series:	-
Reference Type:	External, Internal
Packaging:	Tape & Reel (TR)
Package / Case:	SOT-23-8 Thin, TSOT-23-8
Output Type:	Voltage - Buffered
Operating Temperature:	-40°C ~ 125°C
Number of D/A Converters:	1
Number of Bits:	12
INL/DNL (LSB):	±0.5, ±1 (Max)
Differential Output:	No
Data Interface:	I ² C
Architecture:	-

Related products



LTC2631AHTS8-LM12#TRMPBF
IC DAC 12BIT VOUT TSOT23-8
[Linear Technology](#)

RFQ



LTC2631AITS8-HM12#TRPBF
IC DAC 12BIT VOUT TSOT23-8
[Linear Technology](#)

RFQ



LTC2631AITS8-LM12
[LT](#)

RFQ



LTC2631AHTS8-LZ12#TRMPBF
IC DAC 12BIT VOUT TSOT23-8
[Linear Technology](#)

RFQ



LTC2631AHTS8-LM12#TRPBF
IC DAC 12BIT VOUT TSOT23-8
[Linear Technology](#)

RFQ



LTC2631AITS8-HM12#TRMPBF
IC DAC 12BIT VOUT TSOT23-8
[Linear Technology](#)

RFQ



LTC2631AHTS8-HZ12#TRPBF
IC DAC 12BIT VOUT TSOT23-8
[Linear Technology](#)

RFQ



LTC2631AITS8-HZ12#TRPBF
IC DAC 12BIT VOUT TSOT23-8
[Linear Technology](#)

RFQ



LTC2631AHTS8-LM12
[LT](#)


RFQ



LTC2631AITS8-HZ12#TRMPBF
IC DAC 12BIT VOUT TSOT23-8
[Linear Technology](#)

RFQ

Guess You May Looking For

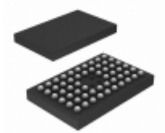

74LVTH162373ZQLR
IC 16BIT TRANS D LATCH 56BGA
[Texas Instruments](#)

RFQ



MM74HC154WMX
IC DECODER 4-16 LINE 24-SOIC
[Fairchild/ON Semiconductor](#)

RFQ



MAX9967ADCCQ+TD
IC DCL DUAL 500MBPS ATE 100TQFP
[Maxim Integrated](#)

RFQ




MC100EP16FDTR2
IC RCVR/DRVR 5V DIFF ECL 8-TSSOP
[ON Semiconductor](#)

RFQ



SN74SSTV16857DGVRG
IC REG BUFF 14BIT SSTL 48-TVSOP
[Texas Instruments](#)

RFQ

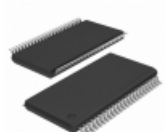

CLVCH16T245MDGVREP
IC TRANSCEIVER 16BIT 48TVSOP
[Texas Instruments](#)

RFQ



AS7C1026B-12TCN
IC SRAM 1MBIT 12NS 44TSOP
[Alliance Memory, Inc.](#)

RFQ




DS1225AD-70IND+
IC NVSRAM 64KBIT 70NS 28EDIP
[Maxim Integrated](#)

RFQ



FM24V10-G
IC FRAM 1MBIT 3.4MHZ 8SOIC
[Cypress Semiconductor Corp](#)

RFQ

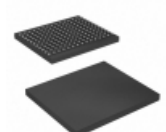

CY7C1312KV18-250BZXC
IC SRAM 18MBIT 250MHZ 165FBGA
[Cypress Semiconductor Corp](#)

RFQ